

## Computer Systems


### Week 3 Assessment Tasks

#### SIT111 - Task 3.1P

By the knowledge of AND, OR, NOT, XOR and HalfAdder gates I used 2 HalfAdders to construct the FullAdder

This FullAdder takes 3 inputs (A,B,C in) and gives 2 outputs as some and carry (S,C)

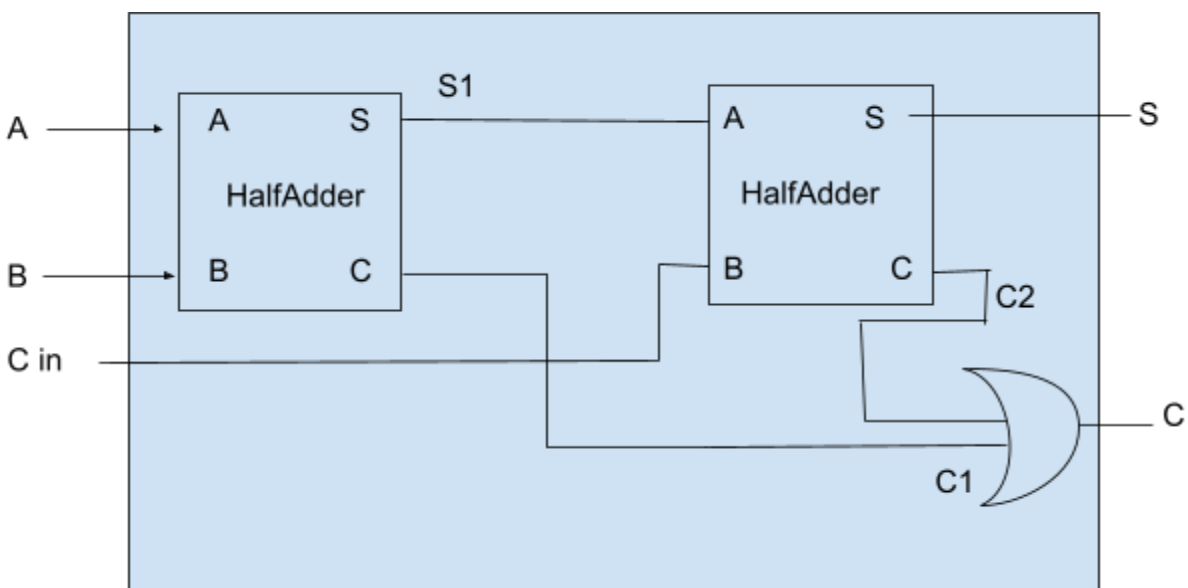**This is the rough diagram (logic circuit) of my FullAdder and the Truth Table**



a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1